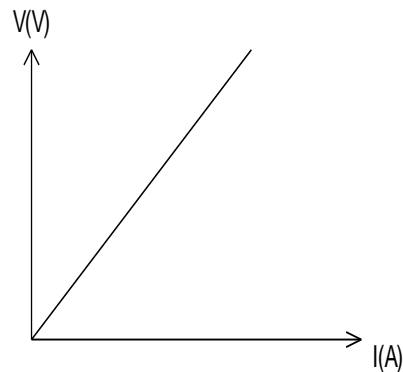


E.5 Ohm's Law

Video: Ohm's Law

In any Circuit, if a circuit element gives a straight line graph of V vs I, as shown



It is said that the element **obeys** Ohm's Law

$$V \propto I$$

$$V = IR$$

R is called the resistance and is measured in Ohms (Ω)

Example

A resistor of 5Ω is supplied with a potential which can vary from 1 V to 100 V.

a What will be the range of current that will flow in it?

b How much energy will be dissipated in the resistor each second when $V = 100\text{V}$?

Solution

a 5 V are required to make 1 A flow in this resistor. Therefore, at 1 V the current will be A or 0.2 A. More formally:

$$\text{At } 1 \text{ V, } I = V/R = 0.2 \text{ A}$$

At 100 V, $I = 20 \text{ A}$ (or simply 100 times the previous answer).

b At 1 V, 0.2 C flow through the resistor each second. The energy is given by:


$$\Delta U = qV$$

$$= 0.2 \times 1$$

$$= 0.2 \text{ J}$$

$$\text{At } 100 \text{ V, } \Delta U = 20 \times 100 = 2000 \text{ J}$$

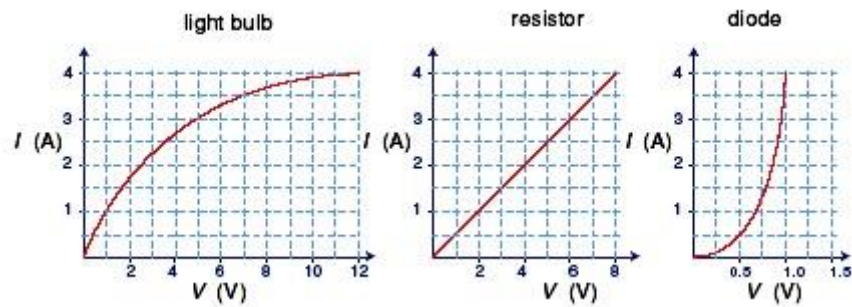
Devices which **do not** have straight lines for their graphs of V vs I are called non-ohmic devices. Examples of these are light globes and diodes.



When working with non-ohmic devices we use the graph to find our information.

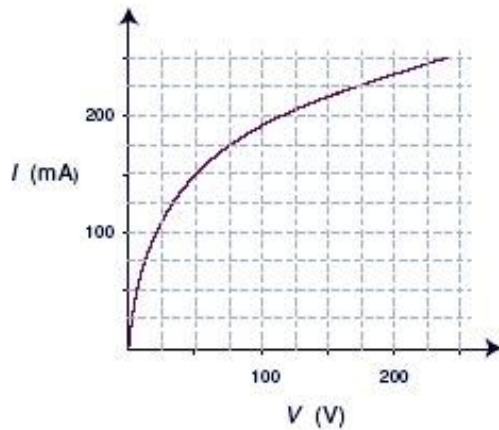Example

The graph represents the $I-V$ characteristic of a 240 V, 60 W light bulb.



What is the resistance at:

- a 24 V?
- b 120 V?
- c 240 V?

Solution

Resistance is given by $R = V/I$ at any point on the graph. Note that the current is given in mA (100 mA = 0.1 A).

a At 24 V

$$R = 24/0.10$$

$$= 240 \Omega$$

b At 120 V

$$R = 120/0.20$$

$$= 600 \Omega$$

c At 240 V

$$R = 240/0.25$$

$$= 960 \Omega$$

E.6 Resistances

A resistor or a resistance is a circuit element that **resists** the flow of electricity (electrons). The higher the number the **higher** the resistance. The units of resistance are Ohms (Ω). Experiments show that the resistance of a metal will depend on its length, area and material.

$\therefore R = \frac{\rho l}{A}$ where ρ is a constant for the material called the resistivity (Ωm).

Problem Set #4: Text Section 3.4 Page 119-120 Questions 1 – 8