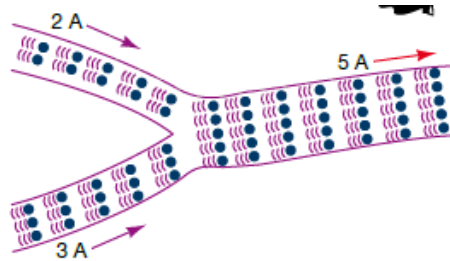


E.7 Circuit Rules


There are two rules for electric circuits, known as Kirchoff's laws. They relate to the conservation of **charge** and conservation of **energy**.

In any electric circuit the sum of all currents flowing into any point is equal to the sum of the currents flowing **out** of it.

For example, if at a junction of three wires there is 2 A flowing in on one wire and 3 A flowing in on another, then there must be a current of 5 A flowing out on the third.



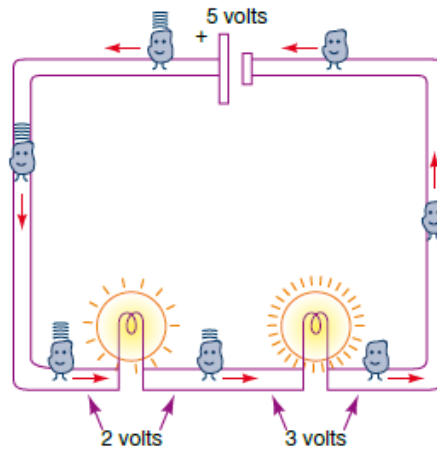
The total potential drop around a closed circuit must be equal to the total EMF in the circuit. In a torch, for example, if the battery supplies an EMF of 3.0 V and we measure a 2.8 V p.d. across the bulb, there must be a 0.2 V drop somewhere else in the circuit.



E.8 Voltage and Current in a Circuit

E.8.1 Series Circuits

Video: Hewitt Drew it – Voltage drop

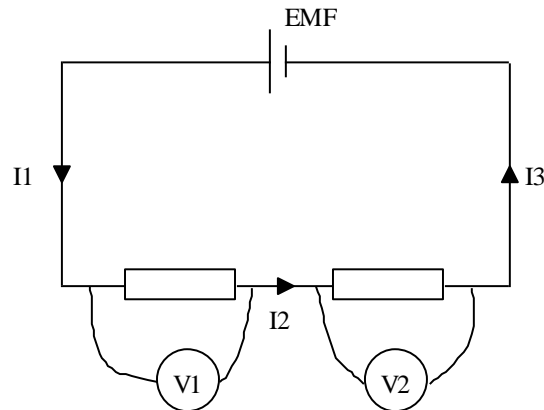

$I_1 = I_2 = I_3$ In series circuits the current remains the **same**

$V_1 + V_2 = \text{E.M.F.}$ In series potential differences **add up**

In a series circuit, the current leaves the battery, travels around the loop of the circuit passing through each circuit element. As the charges move through each circuit element they **transfer/transform** potential (energy) until they arrive back at the battery terminal with **no** electrical energy left. In a series circuit the current is the **same** throughout the circuit.

We can say that the sum of the energies transferred in the circuit = the energy supplied by the battery.

i.e. $\text{EMF} = V_1 + V_2 + V_3 + \dots$

from Ohm's law $V = I R$

we get $I R_T = I R_1 + I R_2 + I R_3 + \dots$

since I is the same around the circuit

$I R_T = I (R_1 + R_2 + R_3 + \dots)$

So $R_T = R_1 + R_2 + R_3 + \dots$

Example

Two pieces of nichrome wire (as used in heater elements) have resistances of $10\ \Omega$ and $20\ \Omega$.

a What current would flow through them, and what power will be produced in them, if they are separately connected to a $12\ \text{V}$ battery?

b If they are connected in series what is their total resistance?

c When placed in series across the $12\ \text{V}$ battery, what current will flow through them and what power will be produced?

Solution

a The current will be given by $I = V/R$, so for the two wires separately the currents will be $12/10 = 1.2\ \text{A}$ and $12/20 = 0.6\ \text{A}$.

The power is found from $P = VI$ and so will be $12 \times 1.2 = 14.4\ \text{W}$ and $12 \times 0.6 = 7.2\ \text{W}$, a total of $21.6\ \text{W}$.

b When connected in series the total resistance will be $10 + 20 = 30\ \Omega$.

c The current that flows from the $12\ \text{V}$ battery will be

$$I = \frac{12}{30} \\ = 0.4\ \text{A}$$

The total power will be $12 \times 0.4 = 4.8\ \text{W}$,