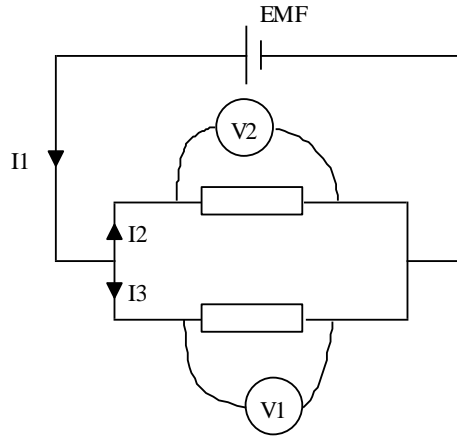


## E.8.2 Parallel Circuits


Video: Hewitt Drew it – Bulbs in parallel



$I_2 + I_3 = I_1$  In parallel the currents **add up**

$V_1 = V_2$  In parallel potential differences are the **same**

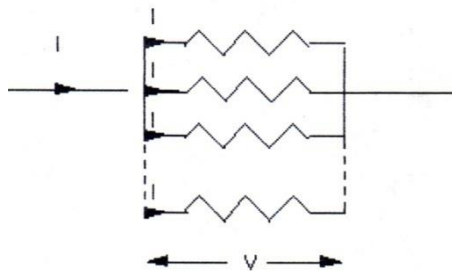In a parallel circuit the current splits up into two or more components while the voltage across each element in the parallel connection is **constant**.



Thus  $I_T = I_1 + I_2 + I_3 + \dots$

From  $V = I R$

$$I = \frac{V}{R}$$

substituting we get

$$\frac{V}{R_T} = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3} + \dots$$

Since V is the same for all resistances

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$$

## Video: Hewitt Drew it – Equivalent Resistance

Example

Two pieces of nichrome wire (as used in heater elements) are found to have resistances of  $10\ \Omega$  and  $20\ \Omega$ .

**a** If they are connected in parallel what is their effective resistance?

**b** What total current will flow through them and what power will be produced if the combination is placed across a  $12\ \text{V}$  battery?

**Solution**

**a** The effective resistance is found from

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$\frac{1}{R_T} = \frac{1}{10} + \frac{1}{20}$$

$$\frac{1}{R_T} = \frac{3}{20}$$

$$\text{Thus } R_T = \frac{20}{3} = 6.7\ \Omega.$$

**b** The total current is given by

$$I = \frac{V}{R}$$

$$I = \frac{12}{6.7}$$

$$= 1.8\ \text{A}$$

The power is therefore

$$P = VI$$

$$= 12 \times 1.8$$

$$= 21.6\ \text{W}$$

**Problem Set #5:** Text Section 4.1 Page 137 All Questions